

KVL: $U_{D1} + E_1 - U_o = 0$

$U_{D1} = U_o - E_1$

D_1 leder ström om $U_o > E_1$

KVL $U_{D2} + U_o + E_2 = 0$

$U_{D2} = -(U_o + E_2)$

D_2 leder ström om $U_o + E_2 < 0 \Rightarrow U_o < -E_2 = -4,0\text{V}$

Fall (1) D_1, D_2 spärrar $-E_2 < U_o < E_1$, $-4,0 < U_o < 6,0\text{V}$

$U_o = U_i \frac{R_L}{R_1 + R_L} = U_i \cdot \frac{1}{2}$

Fall (2) D_1 leder, D_2 spärrar: $U_o = E_1 = 6,0\text{V}$, inträffar då $u_i > 12\text{V}$


Fall (3) D_1 spärrar, D_2 leder: $U_o = -E_2 = -4,0\text{V}$, inträffar då $u_i < -8,0\text{V}$

$u_i(t) = 10 \sin(2\pi t)\text{V}$


$\omega = 2\pi\text{ r/s}$

$f = 1\text{ Hz}$

$T = \frac{1}{f} = 1\text{ s}$

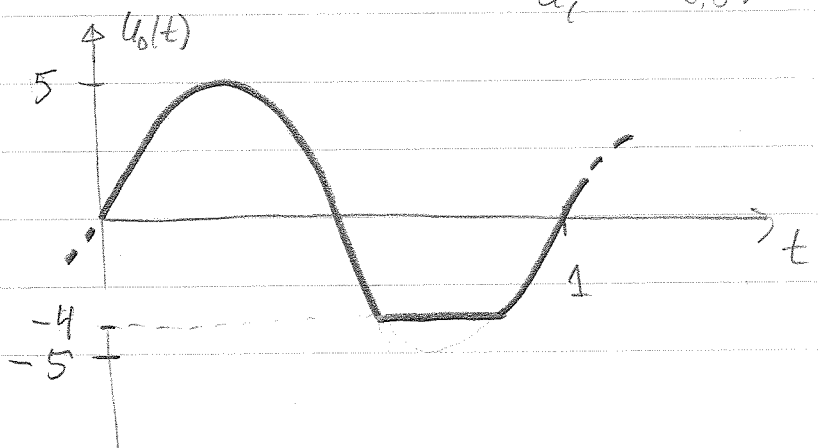

ess115
061220

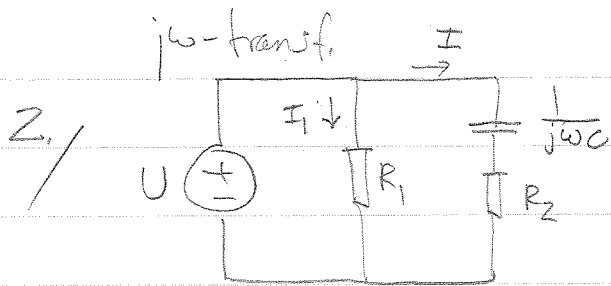

$$u(t) = 15\sqrt{2} \sin(\omega t)$$

$$\omega = 5000 \text{ rad/s}$$

$$\frac{1}{\omega C} = \frac{1}{5000 \cdot 10^{-6}} = 200$$

$$R_1 = 100 \Omega, R_2 = 60 \Omega, C = 1 \mu\text{F}$$

$$I = \frac{U}{R_2 + \frac{1}{j\omega C}} = \frac{15\sqrt{2}}{60 - j200}$$

$$I_1 = \frac{U}{R_1} = \frac{15\sqrt{2}}{100}$$

$$I = \frac{15\sqrt{2} (60 + j200)}{60^2 + 200^2} = \frac{15\sqrt{2} \cdot 10}{43600} (6 + j20) = \frac{15\sqrt{2}}{4360} \sqrt{436} / 73,3^\circ =$$

$$= 0,10 / 73,3^\circ \Rightarrow i(t) = 0,10 \sin(\omega t + 73,3^\circ) \text{ A}$$

Komplex effekt som källan avger (ström ut från plus)


$$S = \frac{1}{2} U (I_1 + I)^* = \frac{1}{2} 15\sqrt{2} \left(\frac{15\sqrt{2}}{100} + \frac{15\sqrt{2} \cdot 10}{43600} (6 - j20) \right) =$$

$$= \frac{1}{2} \frac{(15\sqrt{2})^2}{100} \left[1 + \frac{10}{436} (6 - j20) \right] = \frac{225}{100} \left[1 + \frac{60}{436} - j \frac{200}{436} \right] =$$

$$= 2,25 (1,14 - j0,46) = 2,56 - j1,03 = 2,76 / -22,0 \text{ VA}$$

$$S = P + jQ$$

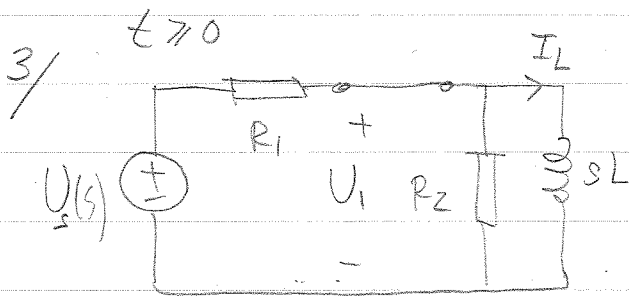Kommentar: $u(t)$ en sinus signal - $j\omega$ metoden utgår ifrån cosinus.
Svaret blir samma om $u(t)$ skrivs om med cosinus



Laplace transformera!
Ingen bes. energi

$$u_s(t) = 30 \cos 5t \xrightarrow{\mathcal{L}} 30 \frac{s}{s^2 + 25}$$

$$U_1 = U_s \frac{R_2 // sL}{R_1 + R_2 // sL} = U_s \frac{\frac{sR_2L}{R_2 + sL}}{R_1 + \frac{sR_2L}{R_2 + sL}} = U_s \frac{sR_2L}{R_1R_2 + sR_1L + sR_2L}$$

$$I_L = \frac{U_1}{sL} = U_s \frac{R_2}{R_1R_2 + sL(R_1 + R_2)} = U_s \frac{\frac{R_2}{L(R_1 + R_2)}}{s + \frac{R_1R_2}{L(R_1 + R_2)}}$$

$$= U_s \cdot \frac{20 / (60 + 20)}{s + \frac{60 \cdot 20}{1 \cdot (60 + 20)}} = U_s \cdot \frac{0,25}{s + 15} = 30 \cdot \frac{s \cdot 0,25}{(s^2 + 25)(s + 15)}$$

$$= \frac{7,5s}{(s^2 + 25)(s + 15)} = \left\{ \begin{array}{l} \text{Partiellbr.} \\ \text{Uppdela} \end{array} \right\} = \frac{As + B}{s^2 + 25} + \frac{C}{s + 15}$$

$$7,5s = (As + B)(s + 15) + C(s^2 + 25)$$


$$\left. \begin{array}{l} s^2: 0 = A + C \\ s^1: 7,5 = 15A + B \\ s^0: 0 = 15B + 25C \end{array} \right\} \text{Lös ekv. systemet} \Rightarrow \begin{array}{l} A = 0,45 \\ B = 0,75 \\ C = -0,45 \end{array}$$

$$I_L = \frac{0,45s}{s^2 + 25} + 0,75 \cdot \frac{1}{s} - \frac{0,45}{s + 15}$$

Inu laplace transf.

$$i_L(t) = \left(0,45 \cos 5t + 0,15 \sin 5t - 0,45 e^{-15t} \right) \cdot \Theta(t) \quad A$$

4. Småsignalschema

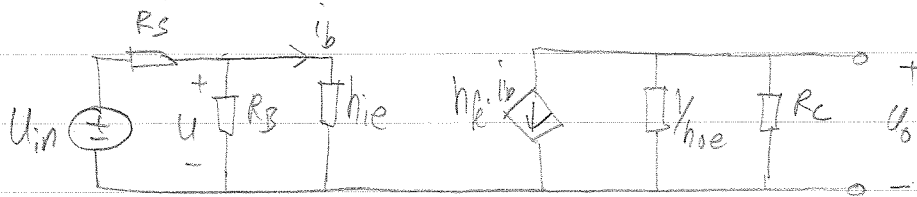

$$U = U_{in} \frac{R_B // h_{ie}}{R_S + R_B // h_{ie}} \Rightarrow U_{in} = U \cdot \frac{R_S + R_B // h_{ie}}{R_B // h_{ie}}$$

$$U = i_b \cdot h_{ie}$$


$$U_o = -h_{fe} \cdot i_b \cdot \left(\frac{1}{h_{oe}} \right) // R_C = -h_{fe} \cdot \frac{U}{h_{ie}} \cdot \frac{\frac{1}{h_{oe}} \cdot R_C}{\frac{1}{h_{oe}} + R_C} = -U \frac{h_{fe}}{h_{ie}} \cdot \frac{R_C}{1 + R_C \cdot h_{oe}}$$

$$\frac{U_o}{U_{in}} = - \frac{U \frac{h_{fe}}{h_{ie}} \cdot \frac{R_C}{1 + R_C \cdot h_{oe}}}{U \cdot \frac{R_S + \frac{R_B h_{ie}}{R_B + h_{ie}}}{\frac{R_B h_{ie}}{R_B + h_{ie}}}} = - \frac{h_{fe}}{h_{ie}} \cdot \frac{R_C}{(1 + R_C h_{oe})} \cdot \frac{R_B h_{ie}}{R_S (R_B + h_{ie}) + R_B h_{ie}}$$

$$\frac{U_o}{U_{in}} = - \frac{150 \cdot 500 \cdot 27 \cdot 10^3}{1,024 \cdot \left[(27 + 0,52) \cdot 10^3 + 27 \cdot 520 \right] \cdot 10^3} = -47,6 \text{ ggr}$$

$$\text{Svar: } \frac{U_o}{U_{in}} = -47,6 \text{ ggr}$$

5.

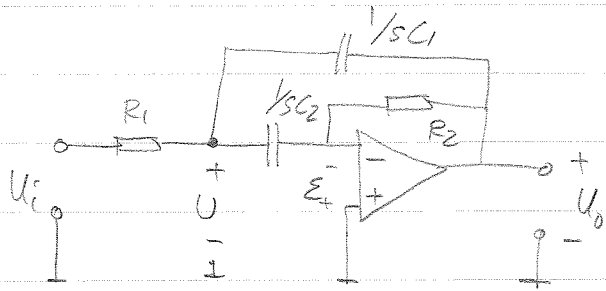

Ideal Op-först. } $\Rightarrow \epsilon = 0$
Neg. återk.
 $i_{op} = 0$

$$\text{KCL: } \begin{cases} \frac{U_i - U}{R_1} + (U_o - U) s C_1 + \frac{U_o}{R_2} = 0 & \Rightarrow \frac{U_i}{R_1} = -U_o \left(s C_1 + \frac{1}{R_2} \right) + U \left(\frac{1}{R_1} + s C_1 \right) \\ U s C_2 + \frac{U_o}{R_2} = 0 & U = -\frac{U_o}{s R_2 C_2} \end{cases}$$

$$\frac{U_i}{R_1} = -U_o \left[\frac{1 + s R_2 C_1}{R_2} + \frac{1 + s R_1 C_1}{R_1} \cdot \frac{1}{s R_2 C_2} \right]$$

$$\frac{U_i}{U_o} = - \left(\frac{R_1}{R_2} (1 + s R_2 C_1) + \frac{1 + s R_1 C_1}{s R_2 C_2} \right) = - \frac{1}{R_2} \left(R_1 + s R_1 R_2 C_1 + \frac{1 + s R_1 C_1}{s C_2} \right)$$

$$= - \frac{s R_1 C_2 + s^2 R_1 R_2 C_1 C_2 + 1 + s R_1 C_1}{s R_2 C_2} = - \frac{s^2 R_1 R_2 C_1 C_2 + s R_1 (C_1 + C_2) + 1}{s R_2 C_2}$$

$$\frac{U_o}{U_i} = - \frac{s / R_1 C_1}{s^2 + s \frac{1}{R_2} \left(\frac{1}{C_1} + \frac{1}{C_2} \right) + \frac{1}{R_1 R_2 C_1 C_2}} = - \frac{s A}{s^2 + s B + \omega_0^2}$$

Svar: Bandpass filter

$$\text{Max först} = \left| \frac{A}{B} \right| = \frac{1}{R_1 C_1} \cdot \frac{R_2 C_1 C_2}{(C_1 + C_2)} = \frac{R_2}{R_1} \cdot \frac{C_2}{(C_1 + C_2)}$$

6.

$$F(s) = \left(\frac{10}{1 + \frac{s}{\omega_1}} \right)^3 \quad \omega_1 = 10^4 \text{ r/s}$$

Studera $\beta F(j\omega)$ $\beta \in \mathbb{R}$

Gränsvfall för instabilitet, $\beta F(j\omega) = -1$

$$\beta F(j\omega) = \frac{\beta 10^3}{\left(1 + j\frac{\omega}{\omega_1}\right)^3} = -1$$

$$\begin{aligned} -\beta 10^3 &= \left(1 + j\frac{\omega}{\omega_1}\right)^3 = \left(1 + j\frac{\omega}{\omega_1}\right) \left(1 + 2\frac{\omega}{\omega_1} - \frac{\omega^2}{\omega_1^2}\right) = \\ &= 1 + j\frac{2\omega}{\omega_1} - \frac{\omega^2}{\omega_1^2} + j\frac{\omega}{\omega_1} - 2\frac{\omega^2}{\omega_1^2} - j\frac{\omega^3}{\omega_1^3} \end{aligned}$$

$$\{\text{Im}\}: \frac{2\omega}{\omega_1} + \frac{\omega}{\omega_1} - \frac{\omega^3}{\omega_1^3} = 0 \Rightarrow 3 = \frac{\omega^2}{\omega_1^2} \quad \omega = \sqrt{3} \omega_1$$

$$\{\text{Re}\}: -\beta 10^3 = 1 - \frac{3\omega^2}{\omega_1^2} = \left\{ \omega = \sqrt{3} \omega_1 \right\} = 1 - 9 = -8 \Rightarrow \beta = 8 \cdot 10^{-3}$$

Amplitudmargin 6dB:

$$|\beta F(j\omega)| = X \quad \text{då} \quad \angle \beta F(j\omega) = -180^\circ \quad \omega = \sqrt{3} \omega_1$$


$$20 \cdot \log X = -6 \Rightarrow X = 10^{-\frac{6}{20}} = 0,5$$

$$|\beta F(j\omega)|_{\omega = \sqrt{3} \omega_1} = 0,5 \Rightarrow \frac{\beta \cdot 10^3}{\left(\sqrt{1 + (\sqrt{3})^2}\right)^3} = 0,5$$

$$\beta_1 = \frac{0,5 \cdot 10^3}{\left(\sqrt{1 + 3}\right)^3} = \frac{0,5 \cdot 10^3}{8} = \frac{\beta}{2} = 4 \cdot 10^{-3}$$

Svar:
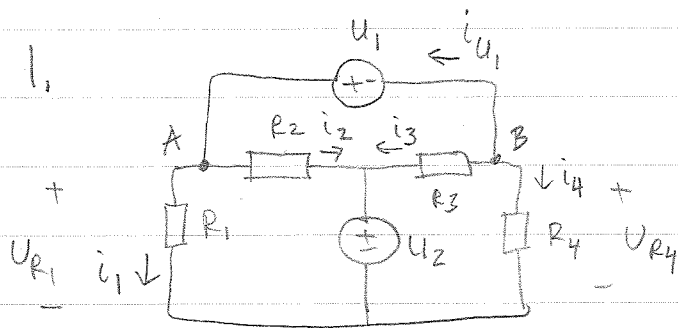
$$\begin{aligned} a) \quad & \beta < 8 \cdot 10^{-3} \\ b) \quad & \beta_1 = 4 \cdot 10^{-3} \end{aligned}$$



$$U_1 = 6.0 \text{ V}$$

$$U_2 = 4.0 \text{ V}$$

$$R_1 = R_2 = 2.0 \text{ k}\Omega$$

$$R_3 = R_4 = 4.0 \text{ k}\Omega$$

$$\left. \begin{array}{l} \text{KCL}_A: \quad i_1 + i_2 - i_{U_1} = 0 \\ \text{KCL}_B: \quad i_3 + i_4 + i_{U_1} = 0 \end{array} \right\} i_1 + i_2 + i_3 + i_4 = 0$$

$$i_1 = \frac{U_{R_1}}{R_1}; \quad i_4 = \frac{U_{R_4}}{R_4}; \quad i_2 = \frac{U_{R_1} - U_2}{R_2}; \quad i_3 = \frac{U_{R_4} - U_2}{R_3}$$

$$\left\{ \begin{array}{l} \frac{U_{R_1}}{R_1} + \frac{U_{R_1} - U_2}{R_2} + \frac{U_{R_4} - U_2}{R_3} + \frac{U_{R_4}}{R_4} = 0 \\ U_{R_1} = U_1 + U_{R_4} \end{array} \right.$$

$$(U_1 + U_{R_4}) \left(\frac{1}{R_1} + \frac{1}{R_2} \right) + U_{R_4} \left(\frac{1}{R_3} + \frac{1}{R_4} \right) = U_2 \left(\frac{1}{R_2} + \frac{1}{R_3} \right)$$

$$U_{R_4} \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right) = U_2 \left(\frac{1}{R_2} + \frac{1}{R_3} \right) - U_1 \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$


$$U_{R_4} = \frac{U_2 \left(\frac{1}{R_2} + \frac{1}{R_3} \right) - U_1 \left(\frac{1}{R_1} + \frac{1}{R_2} \right)}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}} = \frac{4 \left(\frac{1}{2} + \frac{1}{4} \right) - 6 \left(\frac{1}{2} + \frac{1}{2} \right)}{\frac{1}{2} + \frac{1}{2} + \frac{1}{4} + \frac{1}{4}} =$$

$$= \frac{4 \cdot \frac{3}{4} - \frac{24}{4}}{\frac{6}{4}} = -\frac{12}{6} = -2 \text{ V}$$

$$i_4 = \frac{U_{R_4}}{R_4} = \frac{-2}{4 \cdot 10^3} = -\frac{1}{2} \text{ mA}$$

iw-transformera

2.

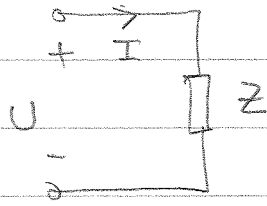

$$|U| = 880 \sqrt{2} \text{ V}$$

$$P = 3,0 \text{ kW}$$

$$Q = 4,0 \text{ kVAR}$$

$$S = P + jQ = \frac{1}{2} U I^*$$

$$U = Z \cdot I \quad \Rightarrow \quad I = \frac{U}{Z}, \quad I^* = \frac{U^*}{Z^*}$$


$$P + jQ = \frac{1}{2} \frac{U U^*}{Z^*} = \frac{1}{2} \frac{|U|^2}{Z^*}$$

$$Z^* = \frac{1}{2} \frac{|U|^2}{P + jQ} = \frac{1}{2} \frac{|U|^2 (P - jQ)}{P^2 + Q^2} \quad \text{och}$$

$$Z = \frac{|U|^2}{2(P^2 + Q^2)} (P + jQ) = \frac{880^2 \cdot 2}{2(3000^2 + 4000^2)} (3000 + j4000) =$$

$$= 92,9 + j124 =$$
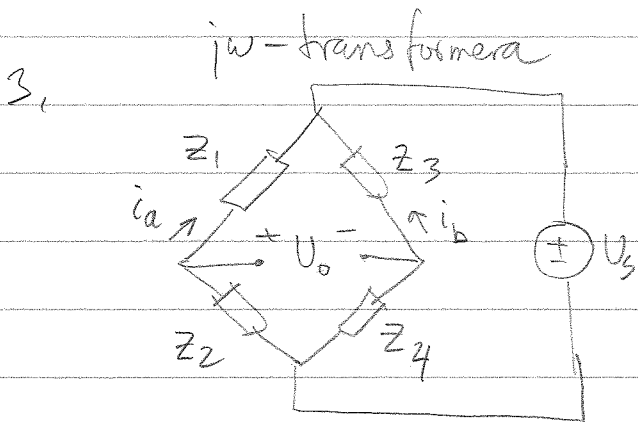
$$= 154,9 \angle 53,1^\circ \quad \Omega$$



$$Z_1 = R_1 // C_1 = \frac{R_1 \frac{1}{j\omega C_1}}{R_1 + \frac{1}{j\omega C_1}} = \frac{R_1}{1 + j\omega R_1 C_1}$$

$$Z_2 = R_2 \quad ; \quad Z_3 = R_3$$

$$Z_x = R_x + j\omega L_x = Z_4$$

$$U_o = 0$$

$$\left. \begin{aligned} \text{KVL: } i_a Z_1 - i_b Z_3 &= 0 \\ -i_a Z_2 + i_b Z_4 &= 0 \end{aligned} \right\} \Rightarrow \begin{aligned} i_a Z_1 &= i_b Z_3 \\ i_a Z_2 &= i_b Z_4 \end{aligned} \Rightarrow \frac{Z_1}{Z_2} = \frac{Z_3}{Z_4}$$


$$Z_x = Z_4 = \frac{Z_2 Z_3}{Z_1} = \frac{R_2 R_3}{R_1} (1 + j\omega R_1 C_1) =$$

$$= \frac{R_2 R_3}{R_1} + j\omega R_2 R_3 C_1 = R_x + j\omega L_x$$

Svar: $R_x = \frac{R_2 R_3}{R_1}$

$$L_x = R_2 R_3 C_1$$

4,

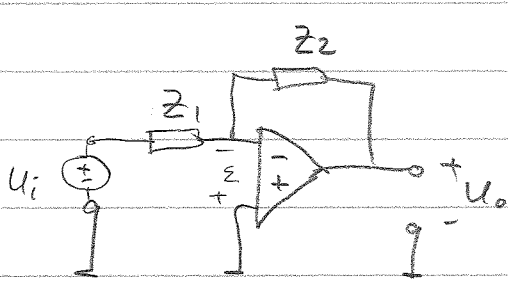

$$Z_1 = R_1 + \frac{1}{j\omega C_1} = \frac{1 + j\omega R_1 C_1}{j\omega C_1}$$


$$Z_2 = R_2 \parallel \frac{1}{j\omega C_2} = \frac{R_2 j\omega C_2}{R_2 + \frac{1}{j\omega C_2}} = \frac{R_2}{1 + j\omega R_2 C_2}$$

Ideal OP-först. + Neg. återkoppling $\Rightarrow \epsilon = 0$

KCL $\frac{U_i}{Z_1} + \frac{U_o}{Z_2} = 0 \quad \frac{U_o}{U_i} = -\frac{Z_2}{Z_1}$

$$\frac{U_o}{U_i} = -\frac{j\omega R_2 C_1}{(1 + j\omega R_1 C_1)(1 + j\omega R_2 C_2)} = -\frac{j\omega R_2 C_1}{(1 + j\frac{\omega}{\omega_1})(1 + j\frac{\omega}{\omega_2})}$$

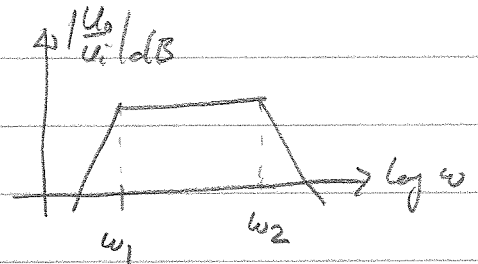Bode diagram (antag $\omega_1 \ll \omega_2$)



Övre gränsvinkel frekvens

$$\omega_2 = \frac{1}{R_2 C_2} = 10^4 \text{ r/s}$$

$$C_2 = \frac{1}{R_2 \cdot 10^4} = \frac{1}{20 \cdot 10^3 \cdot 10^4} = 5,0 \cdot 10^{-9} = 5,0 \text{ nF}$$

Pulsfall $P_{rel} = \Delta t \cdot \omega_1 \cdot 100 = 2 \text{ [\%]}$ $\Delta t = 0,20 \text{ ms}$

$$\Delta t \cdot \frac{1}{R_1 C_1} = 0,02 \quad ; \quad C_1 = \frac{\Delta t}{R_1 \cdot 0,02} = \frac{0,20 \cdot 10^{-3}}{20 \cdot 10^3 \cdot 0,02} = 5 \cdot 10^{-7} =$$

$$= 0,50 \mu\text{F}$$

$$\omega_1 = \frac{1}{R_1 C_1} = 100 \text{ r/s}$$

$\omega_1 \ll \omega_2$ Lågfrekvens och


högfrequ. egenskaper påverkar

ej varandra!


Svar: $C_1 = 0,50 \mu\text{F}$

$C_2 = 5,0 \text{ nF}$

5.

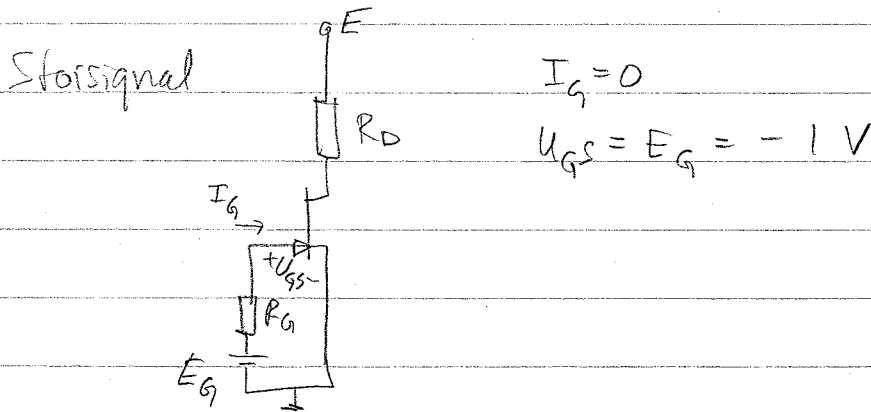

Småsignal

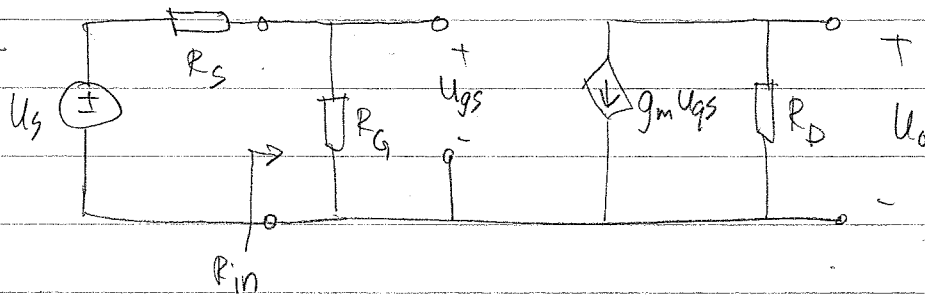

$$U_{gs} = U_s \frac{R_G}{R_s + R_G} \Rightarrow U_s = U_{gs} \frac{R_s + R_G}{R_G}$$

$$U_o = -g_m U_{gs} R_D$$


$$\frac{U_o}{U_s} = - \frac{R_G}{R_s + R_G} \cdot g_m R_D$$

$$g_m = \frac{\partial I_D}{\partial U_{GS}} = \frac{\partial}{\partial U_{GS}} \left(I_{DSS} \left(1 - \frac{U_{GS}}{U_P} \right)^2 \right) = \frac{2 I_{DSS}}{U_P} \left(1 - \frac{U_{GS}}{U_P} \right) =$$

$$= - \frac{2 \cdot 5 \cdot 10^{-3}}{-3} \left(1 - \frac{1}{3} \right) = \frac{10 \cdot 2}{3 \cdot 3} \cdot 10^{-3} = \frac{20}{9} \cdot 10^{-3}$$

$$\frac{U_o}{U_s} = - \frac{100}{10+100} \cdot \frac{20}{9} \cdot 2 = -4,0$$

$$R_{in} = R_G$$

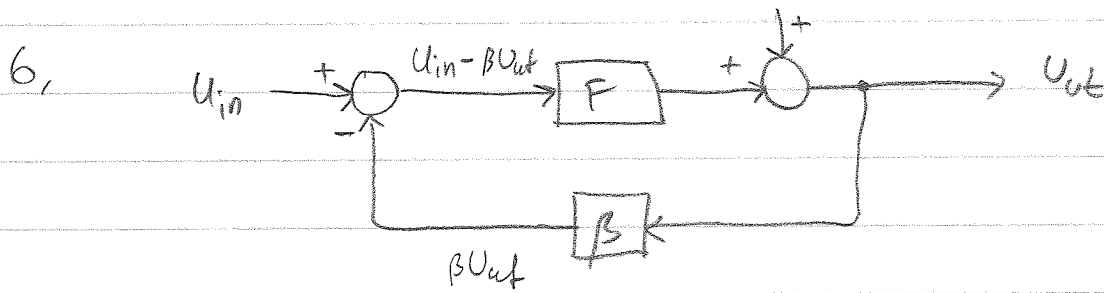

$$U_{out} = U_s + F(U_{in} - \beta U_{out})$$

$$U_{out}(1 + \beta F) = F U_{in} + U_s$$

$$U_{out} = U_{in} \frac{F}{1 + \beta F} + \frac{U_s}{1 + \beta F}$$

Vanligen är $|1 + \beta F| \gg 1$

Stör signal U_s dämpas med faktorn $1 + \beta F$

ESS115 / 070827

$$1/ \quad P_A = -500 \text{ W} \quad Q_A = 866 \text{ VAR}$$

$$P_B = -P_A \quad Q_B = -Q_A$$

Krets A anger
aktiv effekt,
Krets B upptar
aktiv effekt

$$2/ \quad C_1 = 160 \text{ nF} \quad , \quad C_2 = 40 \text{ nF}$$

$$3/ \quad a) \quad i_L = 2,0 \text{ mA} \quad U_o = 5 \text{ V} \quad \text{OK}$$

$$b) \quad i_L = 2,0 \text{ mA} \quad U_o = 8,0 \text{ V} \quad \text{OK}$$

$$c) \quad U_o \text{ "bottnar"} \quad U_o = 9,0 \text{ V} \quad \Sigma \neq 0 \quad i_L = 1,125 \text{ mA}$$

$$4/ \quad U_o(t) = \frac{10}{9} \left(e^{-1000t} - e^{-100t} \right) \cdot \Theta(t)$$

$$5/ \quad \frac{v_o}{v_i} = \frac{g_m \cdot R_L // R_S}{1 + g_m R_L // R_S} = \dots = 0,91$$

$$(R_S = 9,53 \text{ k}\Omega, \quad g_m = 2 \cdot 10^{-3} \text{ A/V})$$

$$6. \quad \angle \beta F = - \left(\arctan \frac{\omega}{\omega_1} + \arctan \frac{\omega}{\omega_2} + \arctan \frac{\omega}{\omega_3} \right) = -150^\circ$$

Passningströkning ger $\omega = 2,2 \omega_1$

$$|\beta F|_{\omega = 2,2 \omega_1} = 1 \quad \Rightarrow \quad \beta = \beta_0 = 0,046$$

$$F_{\text{tot}} = \frac{F}{1 + \beta F} \Big|_{\omega \rightarrow 0} = -18,3$$